

Basic Electrical Engineering

KEE101/201

Department of Engineering
Uttar Pradesh Textile Technology Institute
Session  2019-20
Semester-II
Faculty: Dr Indra Prakash Mishra



Transformers



Text Book

(1) I. J. Nagrath and D. P. Kothari

Basic Electrical Engineering- Tata McGraw Hill

Reference Books:

(2) Alexander S. Langsdorf

Theory of Alternating Current Machinery-TMGH

(3) D. P. Kothari , I. J. Nagrath

Electric Machines-Tata McGraw Hill



Transformer

We understand electrical machines as electro-mechanical energy conversion devices.

Transformer is not really an electro-mechanical energy conversion device

..... It basically converts Voltage!

So first we have to understand.....

.....why voltage transformation is necessary??



Transformer



- The power industry survives on the economics of cost recovery.
- The larger the power plant is, the more economical power generation is.
- Large power plants may be built at the locations where resources like coal or water or gas etc are available in abundance.
- These may be at very far places from the load centers.
- So the power needs to be transported over the long distances from generation stations to load centers.



Why need high Transmission Voltage




- Lines are designed to operate at constant current density J
- $R = \rho \frac{l}{a} = \rho \frac{l}{I} J$
- Transmission Power Loss $P_l = I^2 R$
- Transmission Power Loss $P_l = I^2 \rho \frac{l}{I} J$
- Transmission Power Loss $P_l = I \rho l J$
- Transmission Power Loss $P_l = \frac{P}{V} \rho l J$
- $P_l = \frac{l}{V} X(\text{Constant})$
- So to reduce line loss P_l we need to increase Voltage.



Why need Transformer




- It is not convenient to generate at high voltage say at 400 kV. Generation is normally done at 11 or 22 kV and not more than that.
- Therefore Voltage needs to be stepped up for transmission. 
- It is not convenient and safe to design common load devices which operate at high voltages
- So we need to step down the transmission voltage.
- That's why we need **Transformer !!!!**

Why need Transformer



- Of course the transformer losses come into picture.
- But fortunately we have the transformer efficiency more than 85 % in normal cases.
- So general conception is that we need to have a power system as:


Transformer in Power System

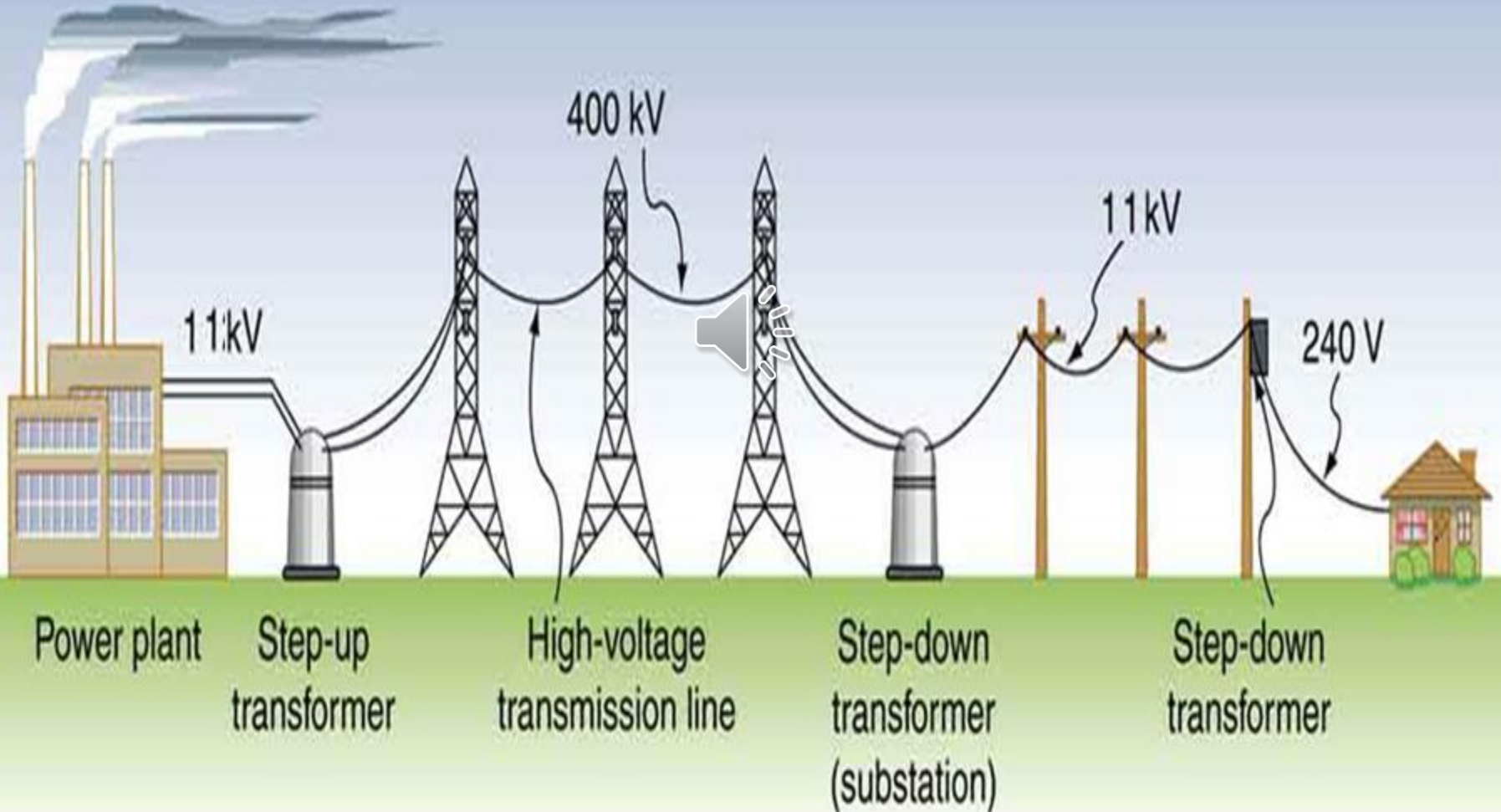

How to transform Voltage ?



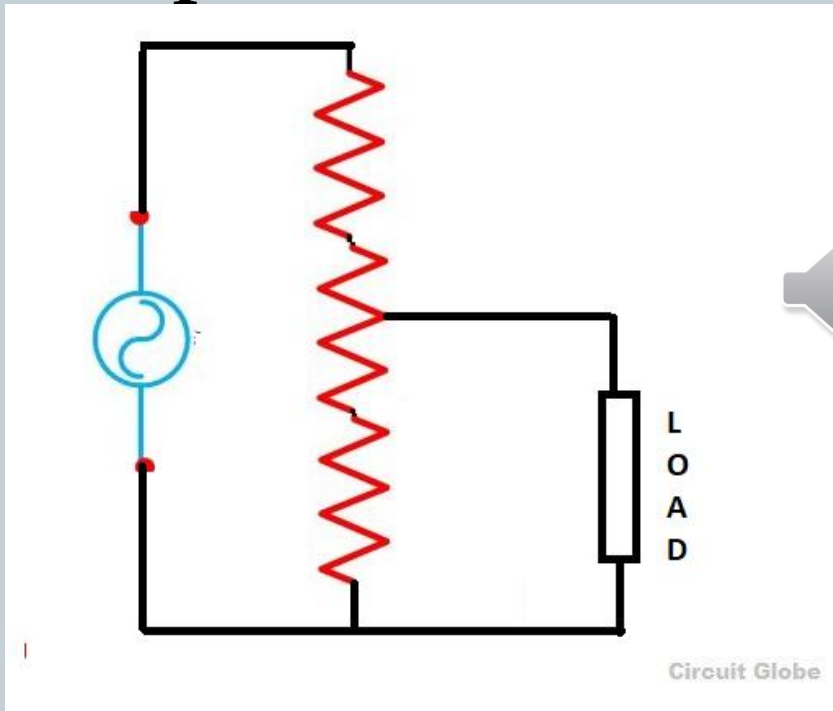- Simplest method is to use potential divider




- But here we cannot step up the voltage
- And there will be huge losses in resistance

How to transform Voltage ?



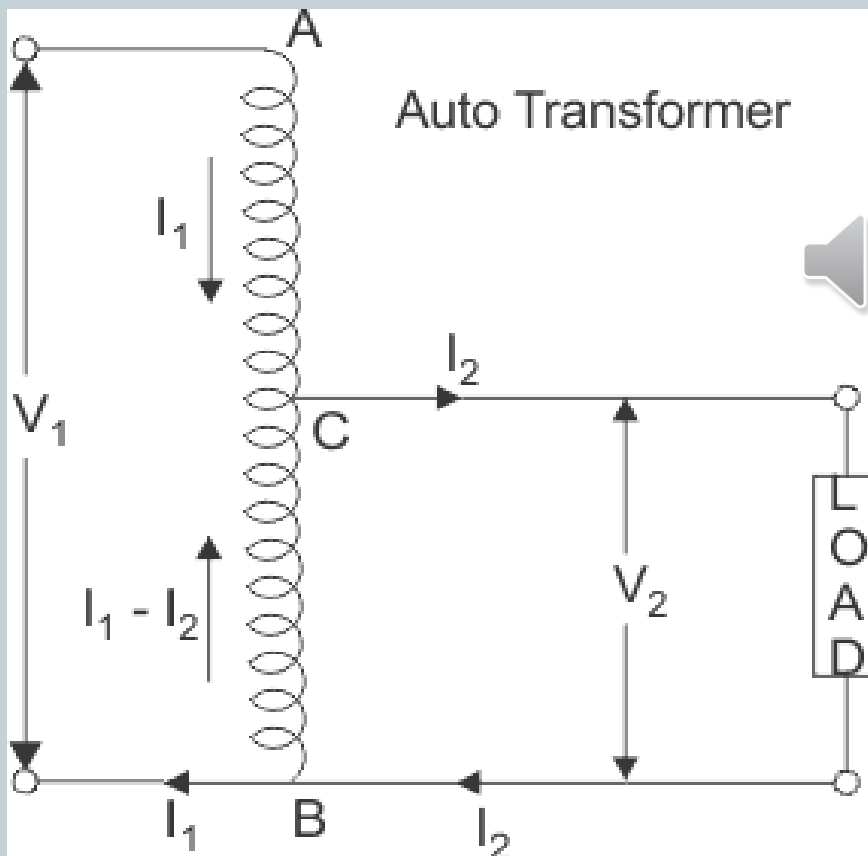- Next option is to use a coil (Inductor)




- Now it is low loss method We may step up the voltage also if we interchange the position of load and source
- possibility of damage to the load during short circuit of A to C or fault.

How to transform Voltage ?



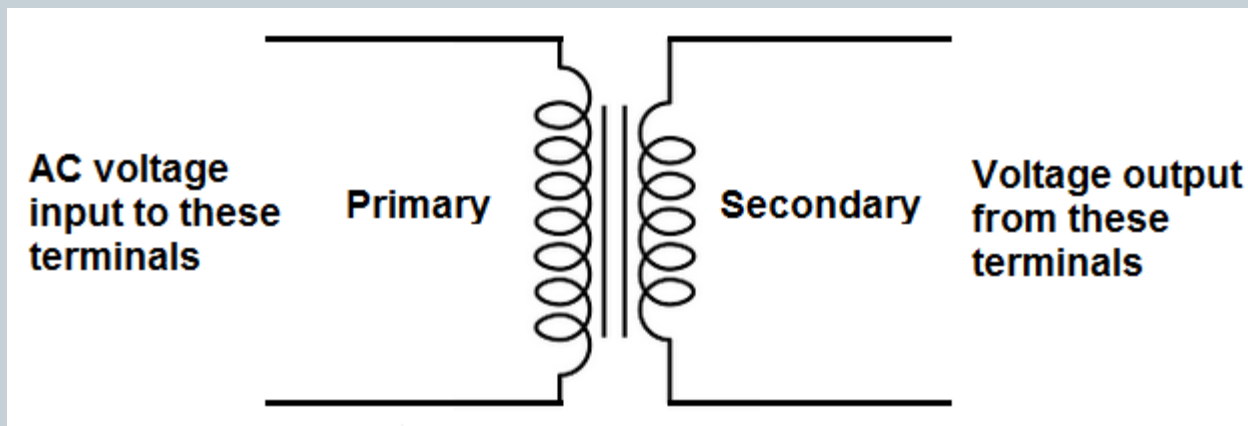- The circuit was basically known as auto transformer.
- Now as magnetic circuits do not need physical connection, we may separate these two coils and couple them magnetically to do the same function.
- Less Probability of Damage to the load during short circuit of two coil terminals.




Magnetic Circuits



AT any point P near to a wire carrying current i :

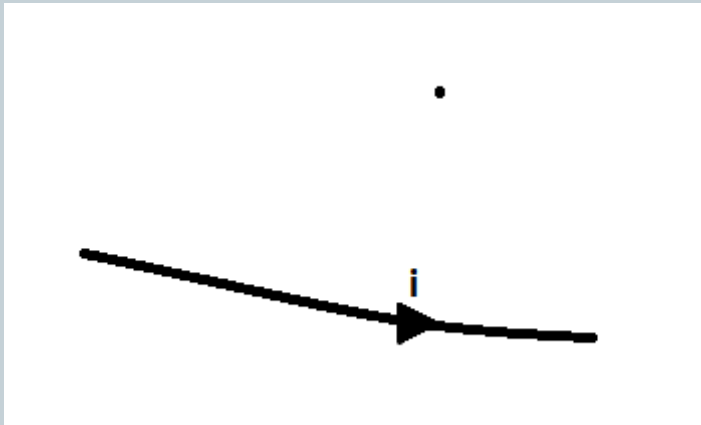- The Magnetic Field intensity vector will be \vec{H} and
- Magnetic flux density vector will be \vec{B}



$$\vec{B} = \mu_r \mu_0 \vec{H}$$


Magnetic Circuits

The Magnetic flux density at the point P due to an incremental length of wire dl will be given by Biot Savart's Law as :

$$d\vec{B} = \frac{\mu_r \mu_o}{4\pi} \frac{id\vec{l} \times \vec{r}}{r^3}$$

$$\vec{B} = \oint \frac{\mu_r \mu_o}{4\pi} \frac{id\vec{l} \times \vec{r}}{r^3}$$

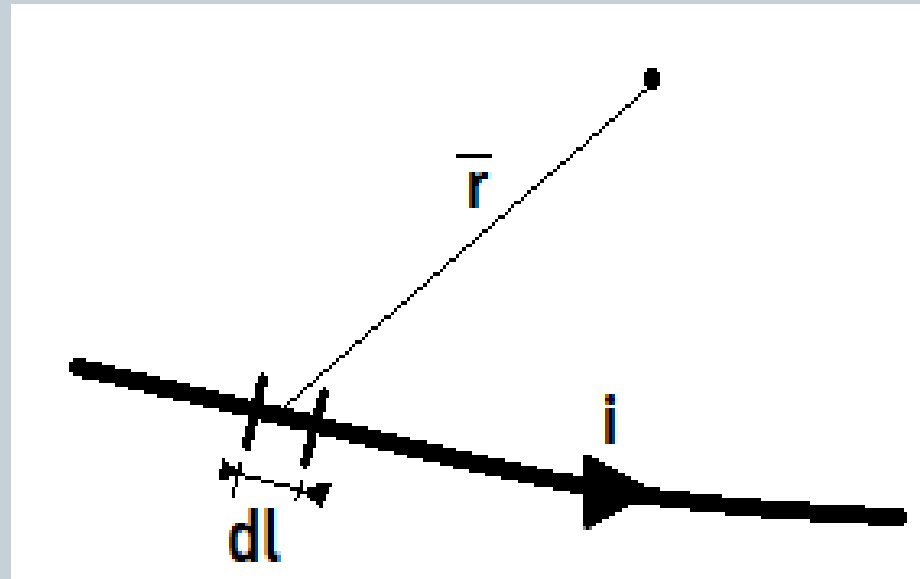The flux density due to wire of length l will be given by the integral over length l .




Magnetic Circuits





- As solution of magnetic circuit using Biot Savart is not convenient we will use another method which is **Amperes Circuital Law**.
- According to this law the Line integral of magnetic field intensity along a closed path will be sum of all the currents enclosed within the loop.

$$\oint \vec{H} \cdot d\vec{l} = I$$

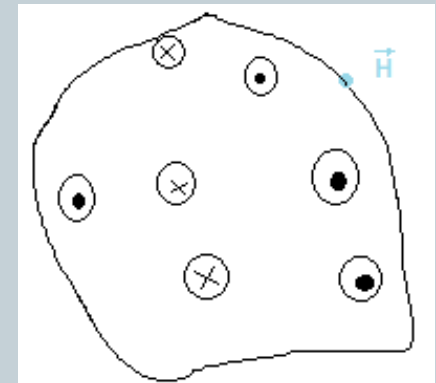

Magnetic Circuits

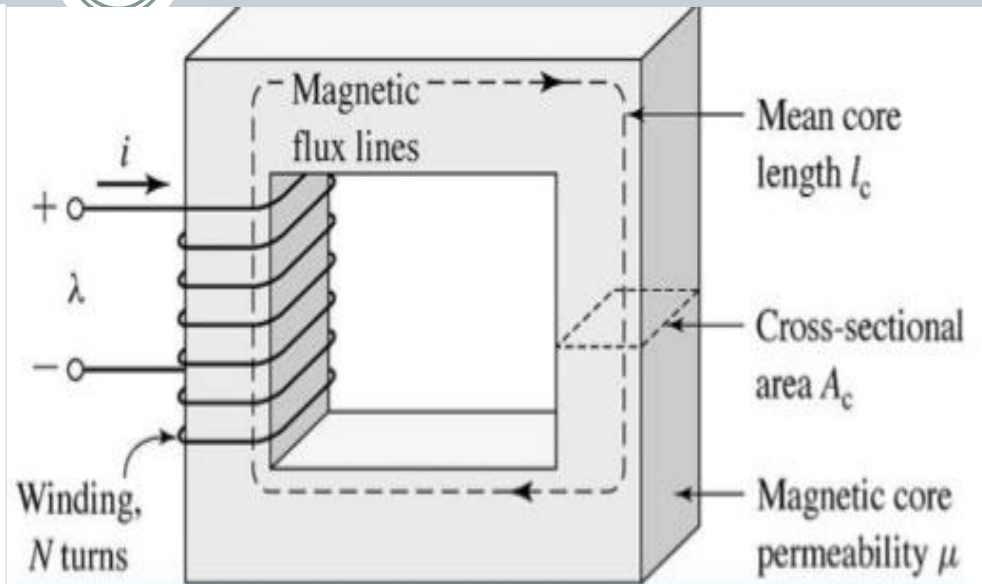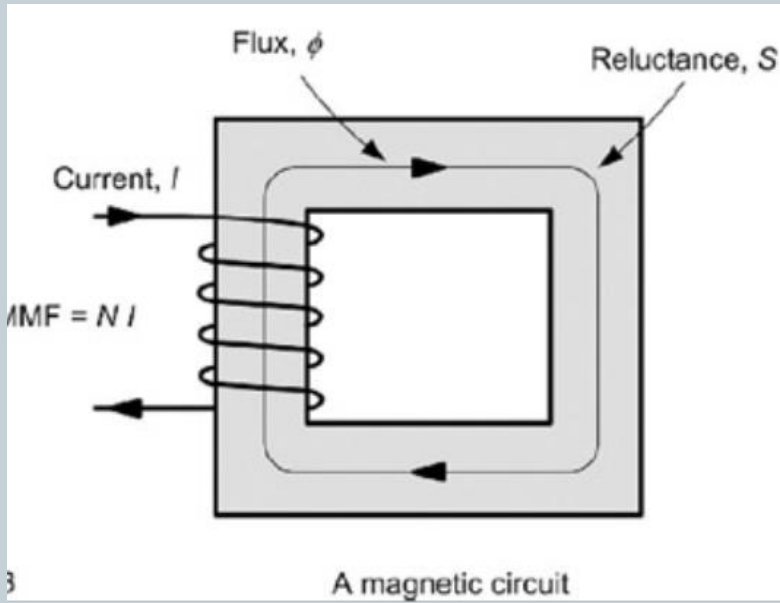

We have a core of regular shape on which some winding is put.

$$\text{Here } N \cdot i = H \cdot l \quad \text{or} \quad H = \frac{Ni}{l}$$


Magnetic Circuits

$$H = \frac{Ni}{l}$$


$$\vec{B} = \mu_r \mu_0 \vec{H}$$

- So finding out B is relatively easier in this way.
- we have assumption that due to high permeability of iron core all the flux is confined to the core
- Hence leakage flux outside the core is negligible

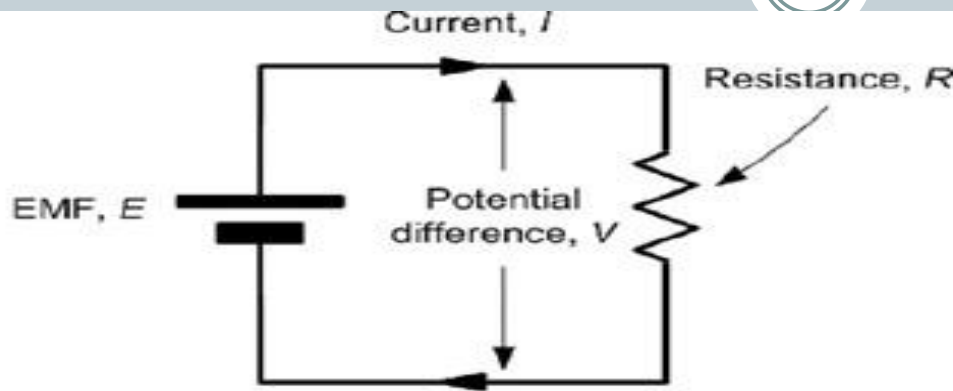Magnetic Circuits : Analogy with Electrical Circuit



An electric circuit

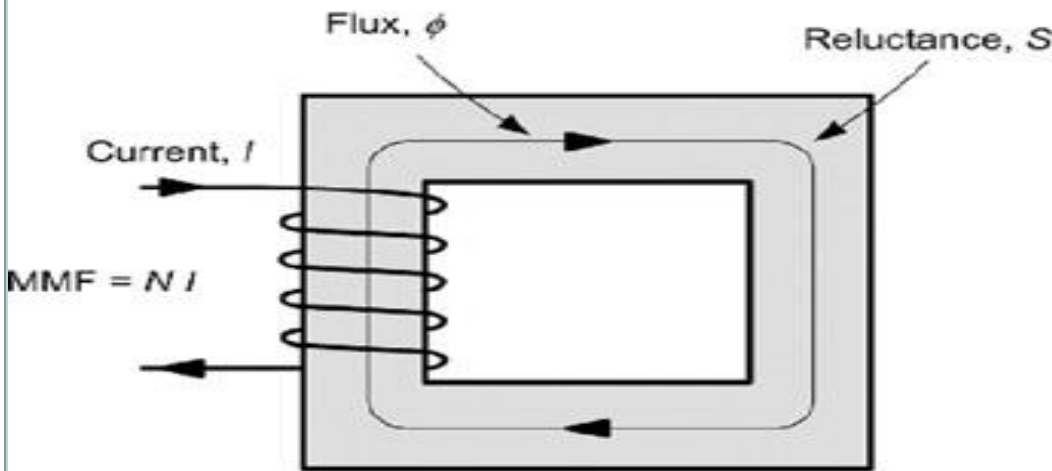

A magnetic circuit

- $\phi = B \cdot A$
- $\phi = \mu_r \mu_0 H \cdot A$
- $\phi = \mu_r \mu_0 \frac{Ni}{l} \cdot A$
- $\phi = \frac{Ni}{\left(\frac{l}{\mu_r \mu_0 A}\right)}$
- $\phi = \frac{Ni}{\mathfrak{R}}$
- $\phi = \frac{MMF}{\mathfrak{R}}$
- $MMF = \phi \cdot \mathfrak{R}$
- Compare with
- $V = I \cdot R$ (Elect Ckt)



will be dc. If ac is applied it will alternate

- Faraday's Law of Electromagnetic Induction:

Emf induced will be equal to the rate of change of flux.

in a coil wound over a

core: $\phi = \phi_m \cos \omega t$

$$e = N \frac{d\phi}{dt}$$

$$e = N\omega\phi_m \sin \omega t$$


$$e = N2\pi f\phi_m \sin \omega t$$

$$E_m = N2\pi f\phi_m$$

$$E_{rms} = \frac{N2\pi f\phi_m}{\sqrt{2}}$$

$$E_{rms} = 4.44f\phi_m N$$

Ideal Transformer

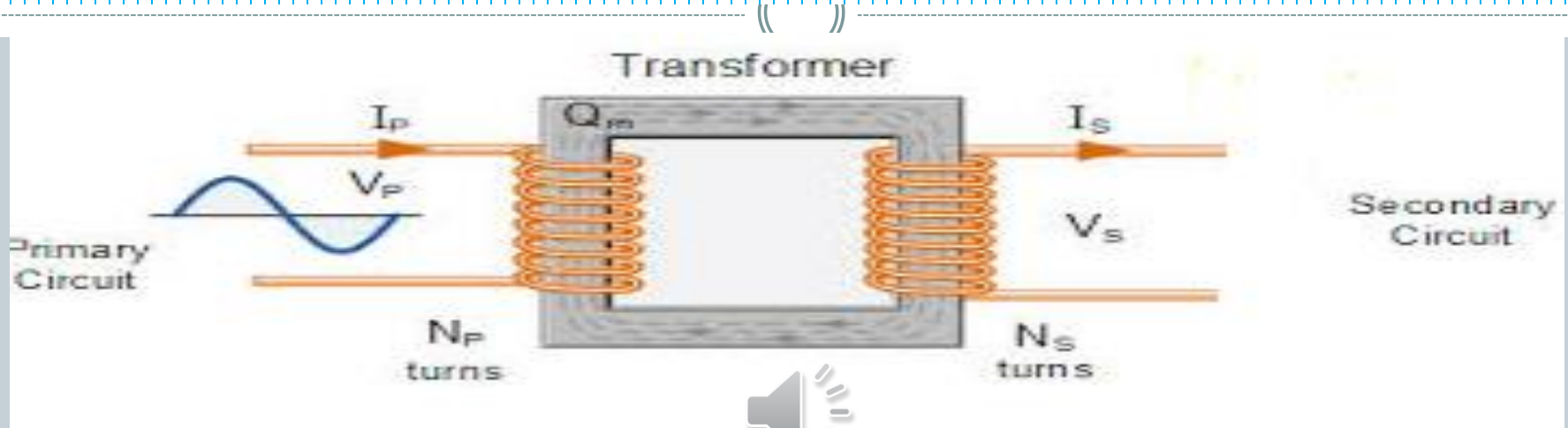


Ideal Transformer is a conceptual Device with following Assumptions:

- Coil resistance is zero (Lossless)
- Core material has infinite permeability
- No flux Leakages (All flux is linked with the core)
- No eddy current losses, No Hysteresis Losses.

Ideal Transformer

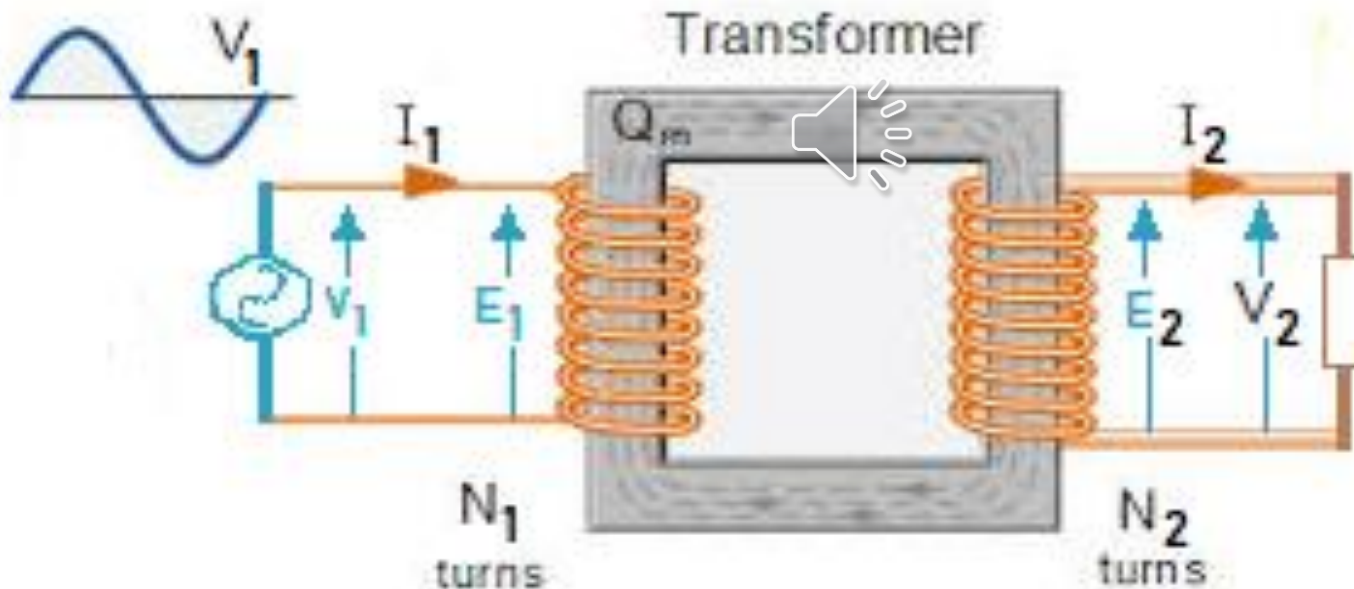Principle of Operation of a conceptual Ideal Transformer





- We must understand that there is no such thing like ‘Ideal Transformer’. It is only a conceptual device.
- If an ac voltage is applied at one side terminals of transformer, This side is known as primary side.
- Another side is called Secondary side.
 - ✦ **Secondary side** : if terminals are left open then transformer is said to be at “No Load”
 - ✦ **Secondary side** : If Load is connected across the terminals the transformer is said to be “On Load”

Ideal Transformer on Load



- $V_1 = \text{Applied ac Voltage (RMS)}$
- $E_1 = 4.44f\phi_m N_1$
- $E_2 = 4.44f\phi_m N_2$
- $E_1 = \text{Induced Voltage in Primary (RMS)}$
- $E_2 = \text{Induced Voltage in Secondary (RMS)}$
- $V_2 = \text{Terminal ac secondary Voltage (RMS)}$
- $\frac{E_1}{E_2} = \frac{N_1}{N_2} = \frac{V_1}{V_2}$

Ideal Transformer on Load



- *Excitation current is zero for primary N_1*
- *$I_2 =$ Secondary current when load is connected*
- *$N_2 I_2 =$ Secondary mmf*
- *$N_1 I_1 =$ Primary counter mmf*
- *$N_2 I_2 = N_1 I_1$*
- $$\frac{N_1}{N_2} = \frac{I_2}{I_1}$$
- **Draw Phasor Diagram**


Ideal Vs Practical Transformer





- Coil resistance is zero (Lossless)
- Core material has infinite permeability
- No flux Leakages (All flux is linked with the core)
- No eddy current losses, No Hysteresis Losses.
- Coil resistance is present though it is low.
- Core material has finite permeability
- Some Flux Leakages occur through air. Represented by Leakage reactance.
- Eddy current and Hysteresis Losses are present. (core or Fixed Losses)



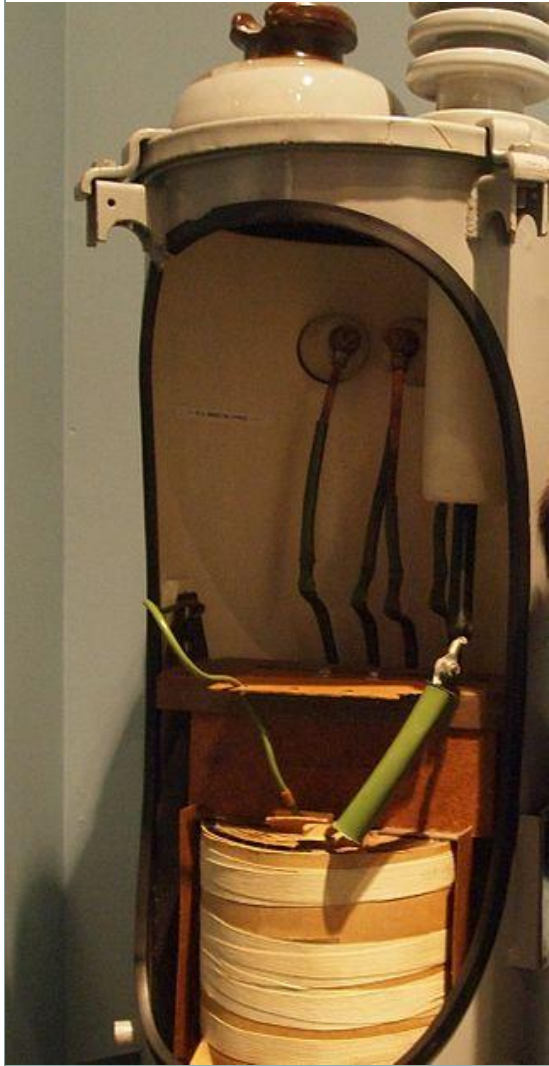
Practical 1-Phase Transformer: Construction



Transformer: Construction

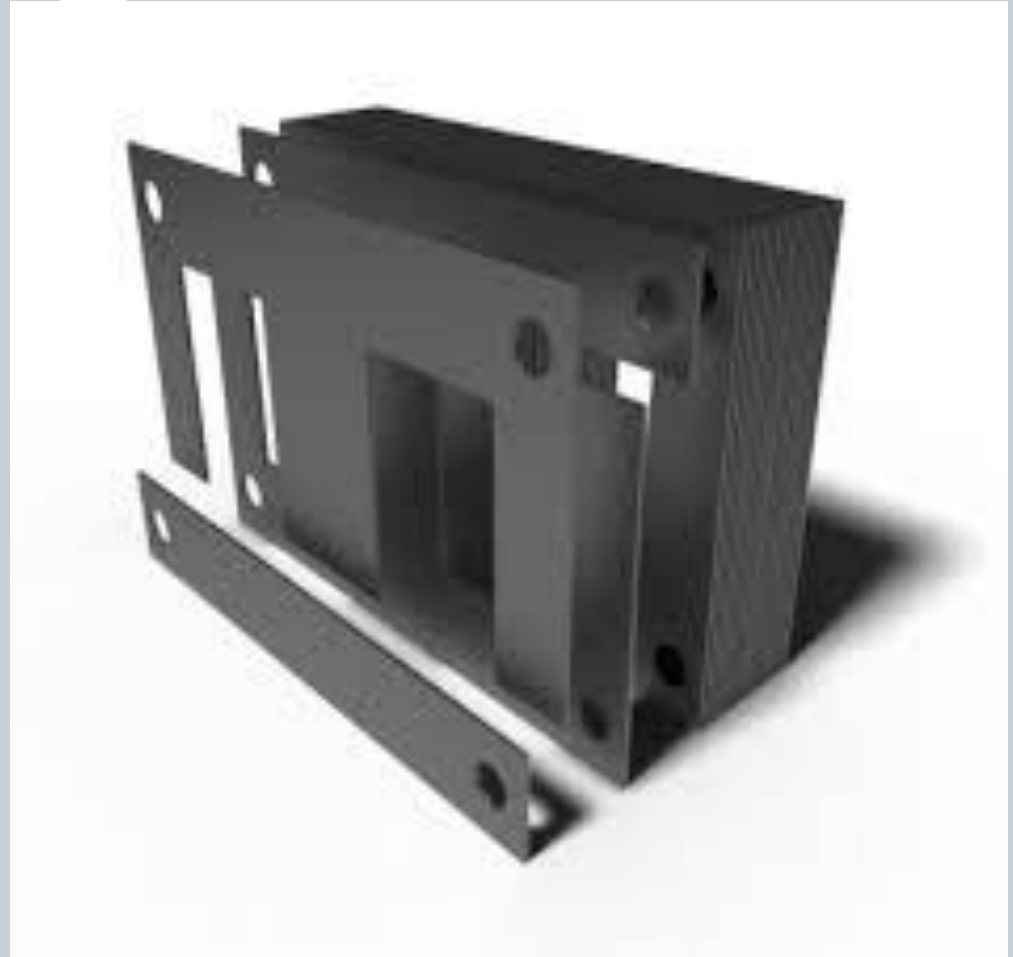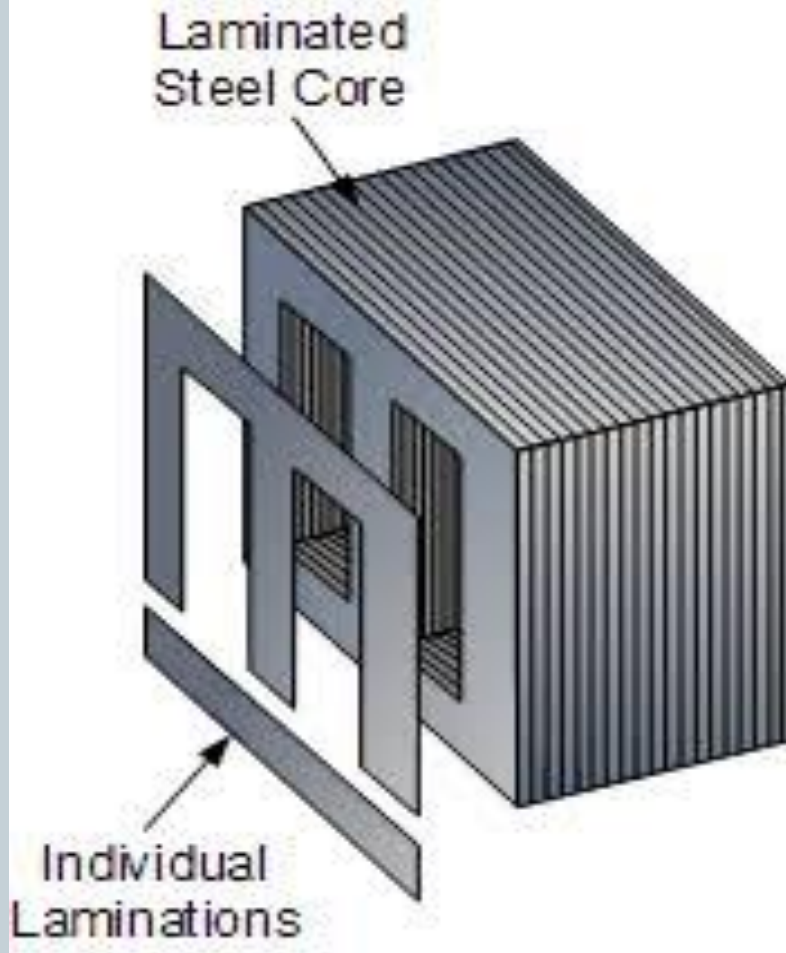

Transformer: Construction

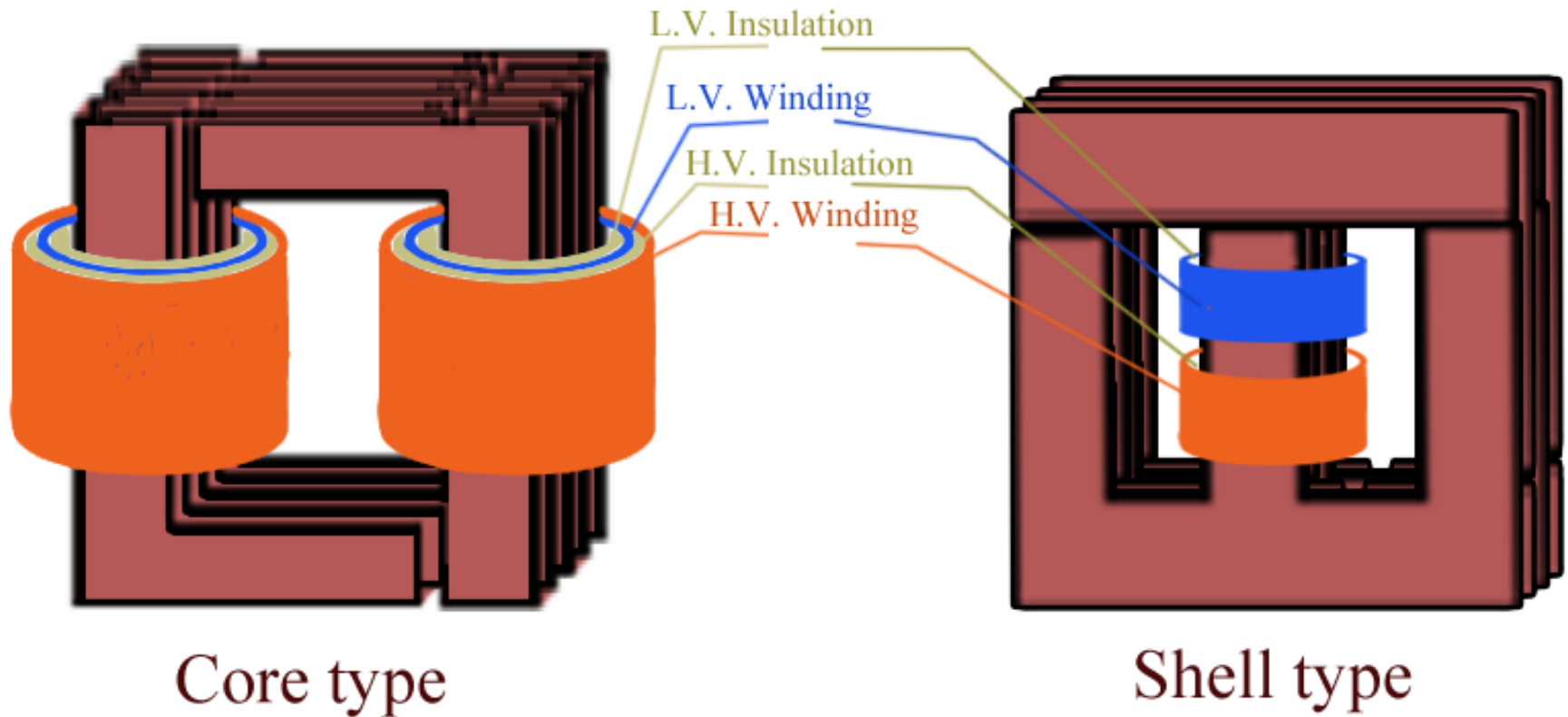

3 Phase Transformer: Construction



