



Quiz 6 Numerical Problems on Transformer

Questions Responses 73

Total points: 20

Section 1 of 2

Quiz 6 Numerical Problems on



Form description

Email address *

Valid email address

This form is collecting email addresses. [Change settings](#)

Name *

Short-answer text

Branch *

Short-answer text

Roll No *

Short-answer text



Short-answer text

After section 1 Continue to next section



Section 2 of 2

Numerical Problems



Description (optional)

The O.C and S.C test data are given below for a single phase, 5 kVA, 200V/400V, 50 Hz transformer. O.C test from LV side : 200V 1.25A 150W, S.C test from HV side : 20V 12.5A 175W. Find Magnetizing component I_m and core loss component, I_c . find magnetizing reactance X_m and core loss resistance R_c referred to LV side. *

Short-answer text

The O.C and S.C test data are given below for a single phase, 5 kVA, 200V/400V, 50 Hz transformer. O.C test from LV side : 200V 1.25A 150W, S.C test from HV side : 20V 12.5A 175W. Find Magnetizing component I_m and core loss component, I_c . find Equivalent leakage reactance X_{eq} and Equivalent Winding resistance R_c referred to hv side. *

Short-answer text

The O.C and S.C test data are given below for a single phase, 5 kVA, 200V/400V, 50Hz transformer. O.C test from LV side : 200V 1.25A 150W, S.C test from HV side : 20V 12.5A 175W. Find Magnetizing component I_m and core loss component, I_c . find Equivalent leakage reactance X_{eq} and Equivalent Winding resistance R_{cu} referred to LV side. *



The O.C and S.C test data are given below for a single phase, 5 kVA, 200V/400V, 50Hz transformer. O.C test from LV side : 200V 1.25A 150W, S.C test from HV side : 20V 12.5A 175W. Calculate the efficiency of the transformer at 75% loading with load power factor = 0.7 *

Short-answer text

.....

The O.C and S.C test data are given below for a single phase, 5 kVA, 200V/400V, 50Hz transformer. O.C test from LV side : 200V 1.25A 150W, S.C test from HV side : 20V 12.5A 175W. Calculate voltage regulation of the transformer at full load with load power factor = 0.7 *

Short-answer text

.....

The O.C and S.C test data are given below for a single phase, 5 kVA, 200V/400V, 50Hz transformer. O.C test from LV side : 200V 1.25A 150W, S.C test from HV side : 20V 12.5A 175W. Calculate the efficiency of the transformer at full load with load power factor = 0.6 *

Short-answer text

.....

