

Quiz (AC Circuits-II)

*Required

1. Email address *

2. Name *

3. Branch *

Mark only one oval.

TC

MMFT

4. Roll No *

5. Mobile No

6. An ac circuit consists of a pure resistance of 20 ohm and is connected to an ac supply of $282.84 \sin 314t$ Calculate the (i) current (ii) power consumed (iii) equation for current and (iv) frequency of supply 1 point

Mark only one oval.

- 10A, 2kW, $14.44 \sin(314t - \pi/2)$, 50 Hz
- 10A, 2kW, $14.44 \sin 314t$, 50 Hz
- 5A, 1450W, $14.44 \sin 314t$, 50 Hz
- 10A, 2000W, $282.84 \sin 314t$, 50 Hz

7. In an ac circuit consists of a pure Inductor the expression for instantaneous power is * 1 point

Mark only one oval.

$$p = -\frac{V_m I_m}{2} \sin 2\omega t$$

Option 1

$$p = \frac{V_m I_m}{2} \sin 2\omega t$$

Option 2

$$p = \frac{V_m I_m}{2} \cos \Phi - \frac{V_m I_m}{2} \cos(2\omega t - \Phi)$$

Option 3

$$p = \frac{V_m I_m}{2} \cos \Phi + \frac{V_m I_m}{2} \cos(2\omega t - \Phi)$$

Option 4

8. In an ac circuit consists of a pure Capacitor the expression for instantaneous power is *

1 point

Mark only one oval.

$$p = -\frac{V_m I_m}{2} \sin 2\omega t$$

Option 1

$$p = \frac{V_m I_m}{2} \sin 2\omega t$$

Option 2

$$p = \frac{V_m I_m}{2} \cos \Phi - \frac{V_m I_m}{2} \cos(2\omega t - \Phi)$$

Option 3

$$p = \frac{V_m I_m}{2} \cos \Phi + \frac{V_m I_m}{2} \cos(2\omega t - \Phi)$$

Option 4

9. In an ac circuit consists of a Resistance and a Capacitor the expression for instantaneous power is * 1 point

Mark only one oval.

$$p = -\frac{V_m I_m}{2} \sin 2\omega t$$

Option 1

$$p = \frac{V_m I_m}{2} \sin 2\omega t$$

Option 2

$$p = \frac{V_m I_m}{2} \cos \Phi - \frac{V_m I_m}{2} \cos(2\omega t - \Phi)$$

Option 3

$$p = \frac{V_m I_m}{2} \cos \Phi + \frac{V_m I_m}{2} \cos(2\omega t - \Phi)$$

Option 4

10. The complex Volt Amperes in a series circuit are (4330-j2500) and the current is (25+j43.3)A. The applied voltage is: * 1 point

Mark only one oval.

25+j43.3

433-j250

86.6+j50

None of the above

11. A non inductive resistor of 10 ohm is in series with a capacitor of $100\mu\text{F}$ across a 250V, 50Hz ac supply. the current taken by the capacitor and power factor of the circuit *

1 point

Mark only one oval.

- 25+j43.3
- 433-j250
- 86.6+j50
- None of the above

12. A non inductive resistor of 10 ohm is in series with a capacitor of $100\mu\text{F}$ across a 250V, 50Hz ac supply. the current taken by the capacitor and power factor of the circuit *

1 point

Mark only one oval.

- $7.49\angle 72.5$ degree A, 0.3
- $2.24+j7.14$, Cos 72.5 degree
- Both Above
- None of the above

13. An impedance coil in parallel with a $100\mu\text{F}$ capacitor is connected across a 200V, 50Hz supply. The coil takes a current of 4A and the power loss in the coil is 600W. the inductance of the coil will be: *

1 point

Mark only one oval.

- 0.2H
- 0.0105H
- 0.105H
- None of the above

14. An impedance coil in parallel with a $100\mu\text{F}$ capacitor is connected across a 200V, 50Hz supply. The coil takes a current of 4A and the power loss in the coil is 600W. the power factor of the circuit is *
- 1 point

Mark only one oval.

- 0.6365
- 0.6010
- 0.5992
- 0.3656

15. In power triangle, P,Q and S are Respectively: *
- 1 point

Mark only one oval.

- Active Power(W), Reactive Power(VA), Apparent Power(VAR)
- Active Power(W), Reactive Power(VAR), Apparent Power(VA)
- Apparent Power(VA), Active Power(W), Reactive Power(VAR),
- Apparent Power(VAR), Active Power(W), Reactive Power(VA),

This content is neither created nor endorsed by Google.

Google Forms